



One Tube Regenerative Receiver as illustrated in *Alfred Morgan's First Book of Radio & Electronics*  
 Note: I subbed in a *6C5* in place of the 6BF6 (different pin out)  
 The "A" supply is 6 VAC, the "B" 67½ VDC. Use 2000 Ohm Phones

